

Development of 10 bit pipeline ADC

Marek Idzik, K. Świentek, T. Fiutowski,
Sz. Kulis, A.K. Prasoon
AGH-UST Kraków


Kraków 12/4/2010

Readout architecture for luminosity detector at ILC



Prototypes in AMS

 0.35 μm


- 8 channels front-end
- 1 channel ADC (no zero suppression)



Preamplifier & PZC & Shaper

 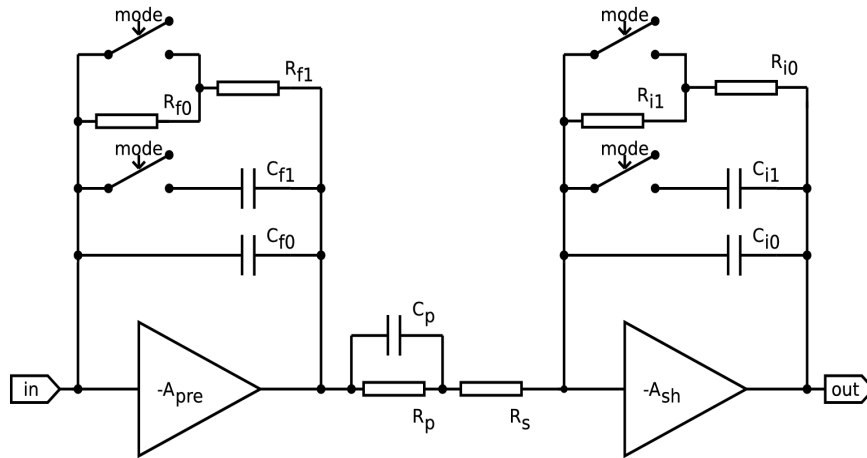

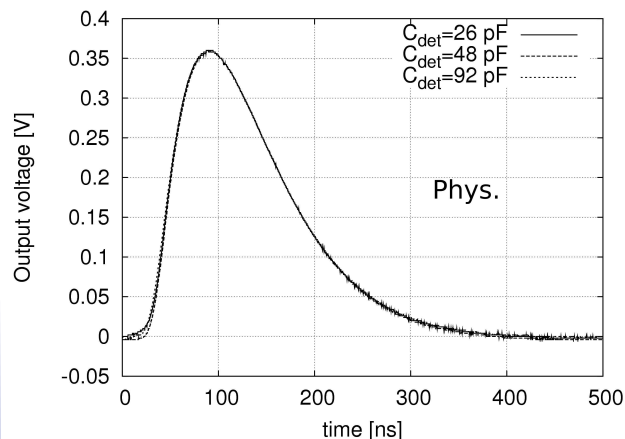
$$\frac{U_{out}(s)}{I_{in}(s)} = \frac{1}{C_f C_i R_s} \cdot \frac{s + 1/C_p R_p}{s + 1/C_f R_f} \cdot \frac{1}{(s + 1/C_i R_i)(s + 1/C_p (R_p \parallel R_s))}$$




- ❑ ASIC with 8 channels
- ❑ Variable gain (MIPs and high input charge up to ~ 10pC)
- ❑ C_{det} range ~ 0-500 pF
- ❑ 1st order shaper $T_{peak} \sim 60$ ns
- ❑ Power consumption < 9 mW/chan³





Design of 10 bit pipeline ADC

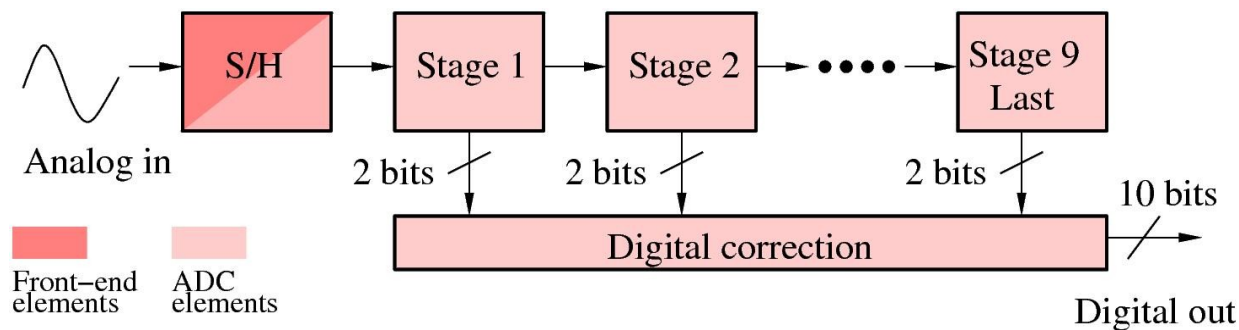

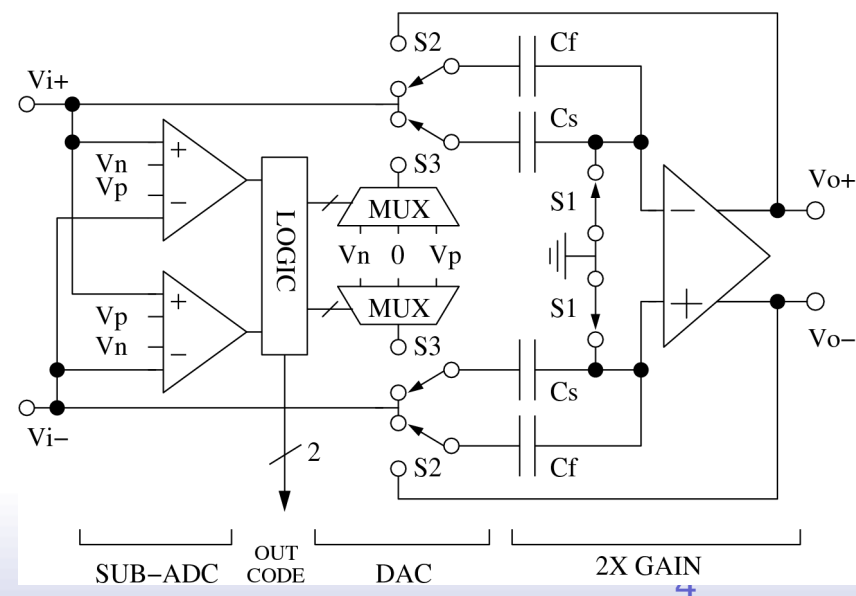- ❑ 10 bit pipeline ADC 1.5 bit/stage
- ❑ Variable sampling frequency up to ~25 Ms/s
- ❑ Scalable power consumption
- ❑ Fully differential
- ❑ Power switching OFF/ON (ILC, CLIC beam timing)
- ❑ Present version in 0.35 μm AMS, smaller size technology soon...




ADC static measurements

    


Very good linearity
INL < 1LSB, DNL < 0.5 LSB

ADC dynamic measurements

 



Good dynamic performance ENOB ~ 9.5 bit

ADC - power OFF/ON

 

Depending on sampling frequency 8-16 clocks needed for switching ON

ADC power consumption

 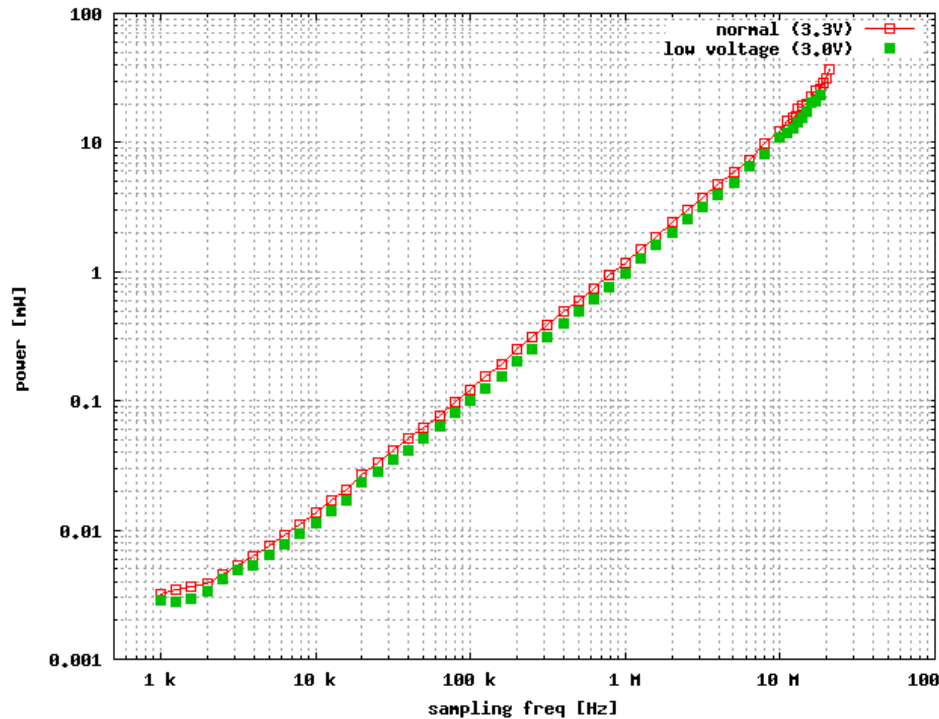

Presently power consumption about 1-1.5 mW/MHz at worst case
(Nyquist input frequency, output buffers)

We have just submitted 8 channels ADC version layout with a pitch
200 μm per channel

Summary

- ❑ ADC fully functional and fulfils the requested specifications
- ❑ A prototype of the multichannel ADC version should be in cracow in a couple of days...
- ❑ Thank you